

Voltage (V)	Current (A)	Power (W)	Energy (J)	Series	Parallel
$v_R = i_R R$	$i_R = \frac{v_R}{R}$	$P_R = \frac{v_R^2}{R} = i_R^2 R$	$E_R = \int_{t_1}^t P_R d\tau$	$R_{eq} = R_1 + R_2 + \dots + R_n$	$R_{eq}^{-1} = R_1^{-1} + R_2^{-1} + \dots + R_n^{-1}$
$v_L = L \frac{di_L}{dt}$	$i_L = \frac{1}{L} \int_{t_1}^t v_L d\tau + i_L(t_1)$	$P_L = Li_L \frac{di_L}{dt}$	$E_L = \frac{1}{2} Li^2$	$L_{eq} = L_1 + L_2 + \dots + L_n$	$L_{eq}^{-1} = L_1^{-1} + L_2^{-1} + \dots + L_n^{-1}$
$v_C = \frac{1}{C} \int_{t_1}^t i_C d\tau + v_C(t_1)$	$i_C = C \frac{dv_C}{dt}$	$P_C = Cv_C \frac{dv_C}{dt}$	$E_C = \frac{1}{2} Cv^2$	$C_{eq}^{-1} = C_1^{-1} + C_2^{-1} + \dots + C_n^{-1}$	$C_{eq} = C_1 + C_2 + \dots + C_n$

Conservation Laws for Voltage, Current, and Power

$\Sigma V_{rise} + \Sigma V_{drop} = 0$ rise: - to +
drop: + to -

$\Sigma I_{in} + \Sigma I_{out} = 0$ in: \rightarrow node
out: \leftarrow node

$\Sigma P_{del} + \Sigma P_{con} = 0$ delivered: - to +
consumed: + to -

Y to Δ Transformation

$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$ $R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$
 $R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$ $R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$
 $R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$ $R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$

$V_S = 0$ Short Circuit \rightarrow
 $I_S = 0$ Open Circuit \rightarrow

Voltage Division

$v_j = \frac{R_j}{R_{eq}} V_S$

Note: R_{eq} is the series resistance equivalent of the circuit, including R_j .

Current Division

$i_j = \frac{R_{eq}}{R_j + R_{eq}} I_S$

Note: R_{eq} is the parallel resistance equivalent of the circuit, not including R_j .

Bridge Circuit

$V_5 = 0$ when $\frac{R_1}{R_2} = \frac{R_3}{R_4}$
 $V_5 = V_1 - V_4$

Thevenin & Norton Equivalents

Thevenin Equivalent
 $V_t = I_{sc} R_{eq}$

Norton Equivalent
 $I_n = \frac{V_t}{R_{eq}}$

Circuit Simplification Methods

$R_{eq} = \frac{V_{oc}}{I_{sc}}$ $R_{eq} = \frac{V_{oc}}{I_{sc}}$ $R_{eq} = \frac{V_{oc}}{I_{sc}}$
 $R_{eq} = \frac{V_{oc}}{I_{sc}}$ $R_{eq} = \frac{V_{oc}}{I_{sc}}$ $R_{eq} = \frac{V_{oc}}{I_{sc}}$

Standard Method for All Sources

- Find V_{oc} for open circuit; $V_t = V_{oc}$
- Find I_{sc} for short circuit.
- Find R_{eq} .

Superposition Method for Independent Sources

- Suppress all independent sources except one and find V_{oc} .
- Repeat step 1 for each independent source that gives you V_{oc} for that particular source.
- Sum all the V_{oc} values to calculate your final V_{oc} .
- Find R_{eq} by removing all sources and using series and parallel simplifications.

Test Source Method for Dependent Sources

- Find V_{oc} for open circuit.
- Insert V_{test} source equal to 1 in open circuit.
- Find I_{test} .
- Find $R_{eq} = \frac{V_{test}}{I_{test}}$.

Natural and Step Responses of RLC Circuits

Overdamped $\alpha^2 > \omega_0^2$
- V or I approaches its final value without oscillation.
- No Overshoot.
 $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$
 $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$
 $x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
 $x(0) = A_1 + A_2$
 $\frac{dx(0)}{dt} = \frac{i_c(0)}{C} = A_1 s_1 + A_2 s_2$

Underdamped $\alpha^2 < \omega_0^2$
- V or I oscillates about its final value.
- Overshoot.
 $s_1 = -\alpha + j\omega_d$
 $s_2 = -\alpha - j\omega_d$
 $x(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$
 $x(0) = B_1$
 $\frac{dx(0)}{dt} = \frac{i_c(0)}{C} = -\alpha B_1 + \omega_d B_2$

Critically Damped $\alpha^2 = \omega_0^2$
- V or I on the verge of oscillating about its final value.
- Almost Overshoots.
 $s_1 = s_2 = -\alpha = -\frac{1}{2RC}$
 $x(t) = (D_1 t + D_2) e^{-\alpha t}$
 $x(0) = D_2$
 $\frac{dx(0)}{dt} = \frac{i_c(0)}{C} = D_1 - \alpha D_2$

Step Response $x(t) = X_f + (OD, UD, CD)$
Natural Response $x(t) = X_f + (OD, UD, CD)$

Characteristic Equation
 $s^2 + 2\alpha s + \omega_0^2 = 0$
Characteristic Roots
 $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$
 $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

$\alpha_p = \frac{1}{2RC}$ Neper/f for RLC Parallel
 $\alpha_s = \frac{R}{2L}$ Neper/f for RLC Series
 $\omega_0 = \frac{1}{\sqrt{LC}}$ Resonant Radian f
 $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ Damped Radian f

V-I Relationships

$V = RI = I_m \angle \theta$ Resistor (V phase I)
 $V = j\omega LI = j\omega LI_m \angle (\theta + 90^\circ)$ Inductor (V leads I)
 $V = \frac{1}{j\omega C} I = \frac{I_m}{\omega C} \angle (\theta - 90^\circ)$ Capacitor (V trails I)

Sinusoidal Steady State

Sinusoidal Form $x = X_m \cos(\omega t + \phi)$
Polar Form $x = X_m \angle \phi$
Phasor Form $x = X_m e^{j\phi}$
 $\sin(\theta) = \cos(\theta - 90^\circ)$ $f = \frac{1}{T}$ $\phi(t=0)$ $\phi_- \rightarrow \times \phi / \omega$
 $\omega = 2\pi f$ $\phi = \Delta t \times \frac{360^\circ}{T}$ $\phi_+ \leftarrow \times \phi / \omega$

NOTE: Δt is the distance between $t = 0$ and the t_f where the closest positive peak amplitude is relative to the vertical axis.

Impedance R(Z)	Reactance j(X)	Admittance R(Y)	Susceptance j(W)
$Z_R = R$	$X_R = -$	$Y_R = G$	$W_R = -$
$Z_L = j\omega L$	$X_L = \omega L$	$Y_L = j(-1/\omega L)$	$W_L = -1/\omega L$
$Z_C = j(-1/\omega C)$	$X_C = -1/\omega C$	$Y_C = j\omega C$	$W_C = \omega C$

- Impedance is the value of resistive measure of that component.
- Admittance is the value of conductive measure of that component.
 $Z = R + jX$ (ohms)
 $Y = G + jW$ (siemens)

Node Voltage Analysis

1. Identify the nodes.
2. Assign ground and circuit variables.
3. Derive equations for independent voltage sources.
4. Derive equations using current law at nodes.
5. Derive equations for dependent sources.

Mesh Current Analysis

1. Identify the meshes.
2. Assign mesh current variables.
3. Derive equations for independent current sources.
4. Derive equations using voltage law for each mesh.
5. Derive equations for dependent sources.

Dot Assignment Method for Mutual Inductance

1. Select one terminal of either coil and mark with a dot.
2. Assign current I_1 into that dot.
3. Use Right-Hand Rule to determine direction of magnetic field ϕ_1 .
4. Select one terminal of the other coil.
5. Assign current I_2 into that terminal.
6. Use Right-Hand Rule to determine direction of magnetic field ϕ_2 .
7. Compare the direction of ϕ_1 and ϕ_2 as follows:
 - If ϕ_1 and ϕ_2 are in the same direction, place the second dot where I_2 enters.
 - If ϕ_1 and ϕ_2 are not in the same direction, place the second dot where I_2 leaves.

RL and RC Circuit Method of Analysis


1. Identify the variable of interest.

$t = \infty$	$t \geq 0$	Time Constants
- For RC, choose V_c	L S.C. I_s	$\tau_L = \frac{L}{R}$
- For RL, choose I_c	C O.C. V_s	$\tau_C = RC$
2. Determine the initial value(s) by drawing circuit at $t = 0$ and solve for R , L , or C equivalent.
 - $t_1: x(0) = x(0) = x(0^+)$
3. Determine the final value(s) by drawing circuit at $t = 0^+$ and $t = \infty$.
 - $t_2: x(\infty) = x(\infty) = x(\infty)$
4. Calculate the time constant. $X(t) = X(\infty) + [X(0) - X(\infty)]e^{-\frac{t-t_1}{\tau}}$


NOTE: R values could be negative if dependent sources are involved.

Operational Amplifiers


Inverting Amplifier

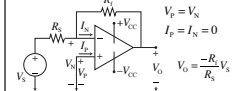


Noninverting Amplifier

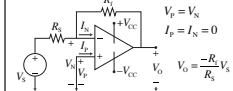

Summing Amplifier

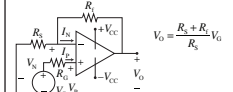


Difference Amplifier

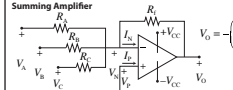


Straight Line Equation

$$(y - y_1) = \frac{y_2 - y_1}{x_2 - x_1} (x - x_1)$$

Example 1

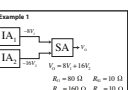

Example 2

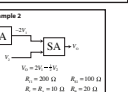

Prefix Symbol Power

Prefix	Symbol	Power
atto	a	10^{-18}
femto	f	10^{-15}
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}
deka	da	10
hecto	h	10^2
kilo	k	10^3
mega	M	10^6
giga	G	10^9
tera	T	10^{12}

Rectangular | Polar | Exponential Conversions

$$a + jb = \sqrt{a^2 + b^2} e^{j\theta}$$

$$ce^{j\theta} = c \angle \theta^\circ \quad \tan^{-1}\left(\frac{b}{a}\right) = \theta^\circ$$

$$ce^{j\theta} = c(\cos \theta + j \sin \theta)$$

$$c \angle \theta^\circ = c(\cos \theta + j \sin \theta)$$

Euler's Identity

$$e^{\pm j\theta} = \cos \theta \pm j \sin \theta$$

Standard Circuit Simplification for One Source

- 1a. If V_s is known, use mesh current analysis to find source current.
- 1b. If I_s is known, use node voltage analysis to find source voltage.
2. Calculate R_{eq} .

Root Mean Square and Power

Converts AC to DC equivalent. $rms = eff$ (effective value)

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2 dt} \quad \text{Apparent Power (VA)} \quad |S| = \sqrt{P^2 + Q^2}$$

$$P_S = -V_{eff} I_{eff}^* = -V_{eff} I_{eff} \angle (\theta_v - \theta_i) \quad X_{eff} = \frac{X_m}{\sqrt{2}} \quad \text{Sine}$$

$$S_S = -V_{eff} I_{eff}^* = -V_{eff} I_{eff} \angle (\theta_v - \theta_i) \quad X_{eff} = X_m \quad \text{Square}$$

$$P = V_{eff} I_{eff} \cos(\theta_v - \theta_i) \quad X_{eff} = \frac{X_m}{\sqrt{3}} \quad \text{Triangle}$$


$$Q = V_{eff} I_{eff} \sin(\theta_v - \theta_i) \quad X_{eff} = \frac{X_m}{\sqrt{3}} \quad \text{Sawtooth}$$

$$P_Z = |I_{eff}|^2 Z = \frac{|V_{eff}|^2}{Z} \quad X_{eff} = \frac{X_m}{\sqrt{3}}$$


$$P_Z = |I_{eff}|^2 R = \frac{I_m^2 R}{2} \quad Q_Z = |I_{eff}|^2 X = \frac{I_m^2 X}{2}$$

$$P_Z = \frac{|V_{eff}|^2}{R} = \frac{V_m^2}{2R} \quad Q_Z = \frac{|V_{eff}|^2}{X} = \frac{V_m^2}{2X}$$

Impedance Graph

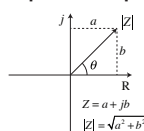

Power Graph

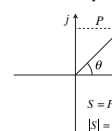

Power for Sinusoidal Steady-State

Average (Real) Power (W), Energy Released $P = \frac{V_{eff} I_{eff}}{2} \cos(\theta_v - \theta_i)$

$$Q = \frac{V_{eff} I_{eff}}{2} \sin(\theta_v - \theta_i)$$

$$S = P + jQ = \frac{V_{eff} I_{eff}}{2} \angle (\theta_v - \theta_i)$$

$$P_s = \frac{V_{eff} I_{eff}}{2} \quad Q_s = - (V \text{ phase } I) \quad p = \pm vi$$

$$P_L = -Q_L \sin 2\omega t \quad Q_L = \frac{V_{eff} I_{eff}}{2} \quad (V \text{ leads } I \text{ by } 90^\circ)$$

$$P_C = -Q_C \sin 2\omega t \quad Q_C = -\frac{V_{eff} I_{eff}}{2} \quad (V \text{ trails } I \text{ by } 90^\circ)$$

$$pf = \cos(\theta_v - \theta_i) \quad rf = \sin(\theta_v - \theta_i)$$

$$NOTE: \text{ If } \theta_v \text{ is greater than } \theta_i, \text{ then } pf \text{ is lagging. If } \theta_v \text{ is less than } \theta_i, \text{ then } pf \text{ is leading.}$$

Maximum Power Transfer

The maximum transfer of power between the source components and the load components is achieved when...



$$Z_L = Z_{Th}^* \quad R_L = R_{Th}$$

If the magnitude of Z_L can be varied but its phase angle cannot, maximum transfer of power to the load is...


$$|Z_L| = |Z_{Th}|$$

NOTE: If one component is set as a variable component, the other component will achieve maximum power when the variable component is set to zero.

$$P_{max} = \frac{|V_{eff}|^2}{4R_L} = \frac{V_m^2}{8R_L}$$

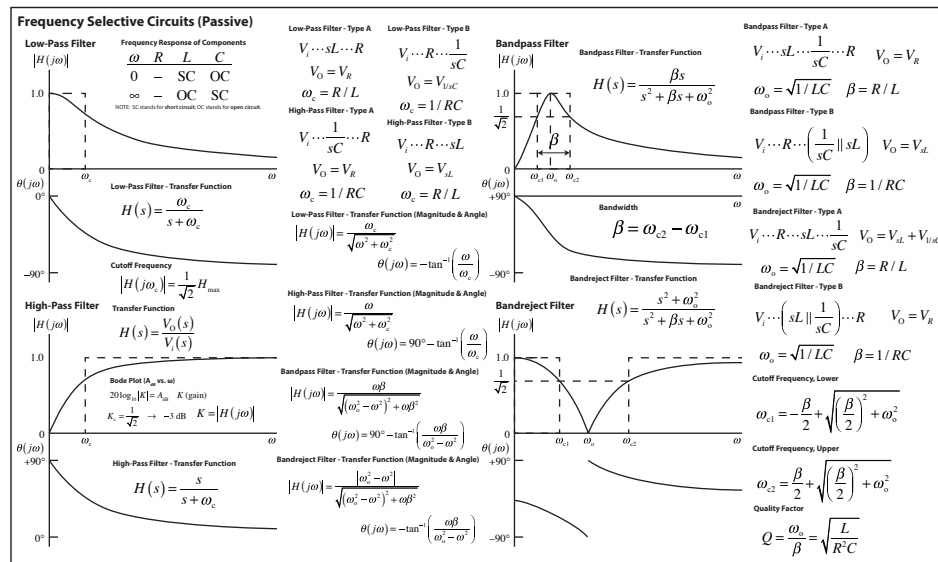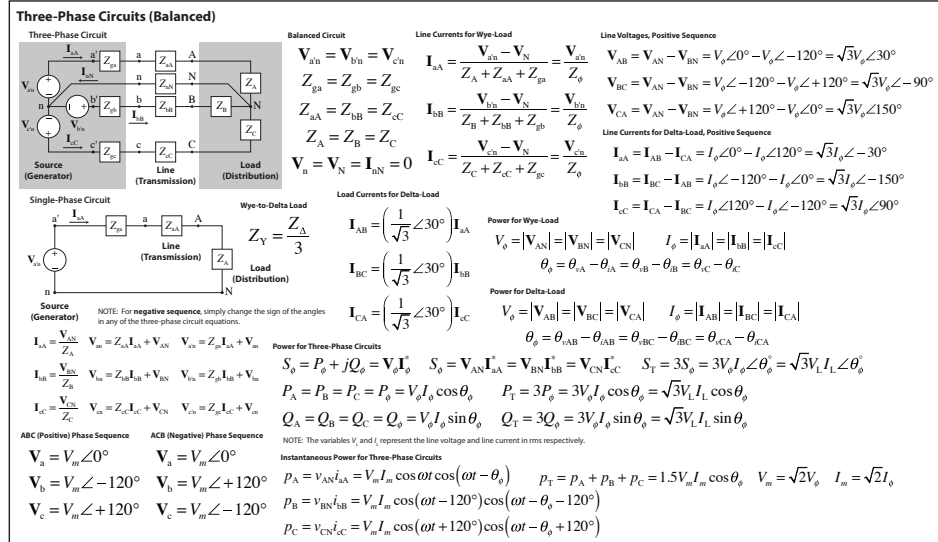

Transformers

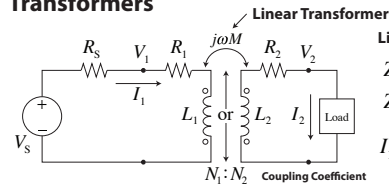

Linear Transformer Laws

$$Z_{11} = R_s + R_1 + j\omega L_1$$

$$Z_{22} = R_2 + j\omega L_2 + R_L$$

$$I_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$

Reflected Impedance

$$Z_r = \frac{\omega^2 M^2}{R_2 + R_L + j(\omega L_2 + X_L)}$$

$$Z_r = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j(\omega L_2 + X_L)]$$

$$|Z_{22}|^2 = (R_2 + R_L)^2 - (\omega L_2 + X_L)^2$$

Ideal Transformer Laws $k = 1$

$$(9.76) \quad \frac{V_L}{V_s} = \pm \frac{V_L}{V_s} \quad \frac{V_1}{N_1} = \pm \frac{V_2}{N_2}$$

$$(9.77) \quad I_s I_s = \pm I_L I_L \quad I_1 N_1 = \pm I_2 N_2$$

Impedance Matching

$$Z_{11} = \frac{V_1}{I_1} = \frac{1}{a^2} \frac{V_2}{I_2} \quad a = \frac{N_2}{N_1}$$

NOTE: L_{sc} and L_{oc} is the inductor in the source loop when the other inductor is in the load loop.


Dot Assignment Rules

Assuming all currents are referenced as clockwise:

- If the dots are diagonal from each other, then M is positive.
- If the dots are across from each other, then M is negative.
- If the coil voltages V_1 and V_2 are both positive or negative at the dot-marked terminal, then Eq. 9.76 is positive; otherwise negative.
- If the coil currents I_1 and I_2 are both directed into or out of the dot-marked terminal, then Eq. 9.77 is negative; otherwise positive.

Frequency Selective Circuits (Active)


Low-Pass Filter

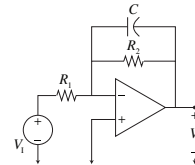

$$H(s) = -K \frac{\omega_c}{s + \omega_c} \quad K = \frac{R_2}{R_1}$$

$$\omega_c = \frac{1}{R_2 C} \quad \omega_c = 2\pi f_c$$


High-Pass Filter

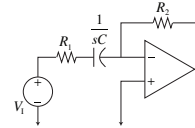

$$H(s) = -K \frac{s}{s + \omega_c} \quad K = \frac{R_2}{R_1}$$

$$\omega_c = \frac{1}{R_1 C} \quad \omega_c = 2\pi f_c$$


Bandpass Filter

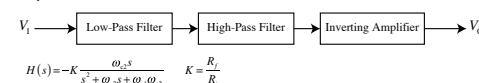

$$H(s) = -K \frac{\omega_c s}{s^2 + \omega_{c1}s + \omega_c \omega_{c2}} \quad K = \frac{R_f}{R_i}$$

$$\omega_{c1} = \frac{1}{R_1 C_H} \quad \omega_{c2} = \frac{1}{R_2 C_L}$$

Bandreject Filter

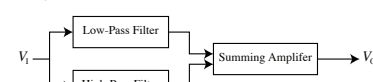

$$H(s) = K \frac{s^2 + 2\omega_c s + \omega_{c1}\omega_{c2}}{(s + \omega_{c1})(s + \omega_{c2})} \quad K = \frac{R_f}{R_i}$$

$$\omega_{c1} = \frac{1}{R_1 C_1} \quad \omega_{c2} = \frac{1}{R_2 C_2}$$

Higher Order Active Filters

Order	Slope
1	± 20 dB/dec
2	± 40 dB/dec
3	± 60 dB/dec
4	± 80 dB/dec

NOTE: The order of the filter is determined by the number of LFP and HPF used which in turn are connected in series to increase the slope of the cutoff frequency.

Example: A Bandpass Filter with two LFP and two HPF is therefore a second-order filter.

Scaling

$$\begin{aligned} R' &= k_m R & L' &= k_m L & C' &= C / k_m \\ R' &= R & L' &= L / k_f & C' &= C / k_f & k_f &= \frac{\omega_c'}{\omega_c} \\ R' &= k_m R & L' &= \frac{k_m}{k_f} L & C' &= \frac{1}{k_m k_f} C \end{aligned}$$

Broadband Filter

$$\frac{\omega_{c2}}{\omega_{c1}} \geq 2$$

Bode Plot (Low-Pass Filter)

