

Figure 8.1: Overdamped $R_1 = 10\text{ k}\Omega$

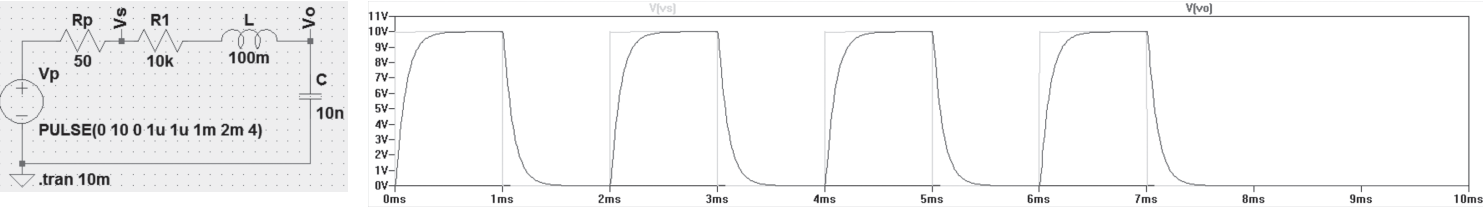


Figure 8.1: Underdamped $R_1 = 500\ \Omega$

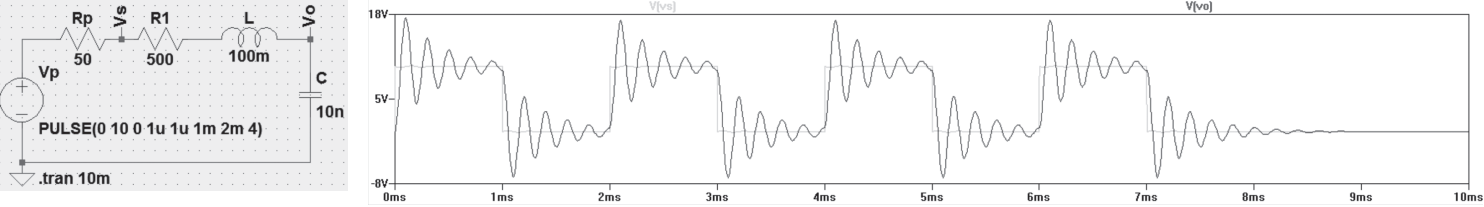


Figure 8.1: Critically Damped $R_1 = 6.3246\text{ k}\Omega$

